



Notes:

U2,U3 are MC33078. One may substitute any standard op amp such as TL082, RC4458, TSH22, or even use a couple of 741's if you're cheap.

C8: Select a capacitor that is as close as you can get to 8nF. I used a 4.7nF in parallel with a 3.3nF

The +15V supply may not be available to many people, however, just get a DC wall-wart that sources anything above 18V up to about 30V and use an LM7815 regulator to get the desired 15V.